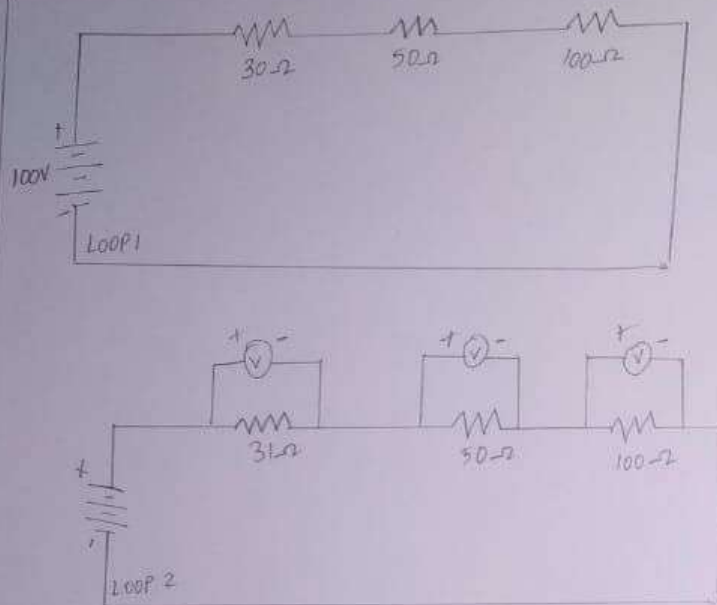


### CIRCUIT DIAGRAM:



### TABULATION:

| KVL         | SOURCE (V) | $V_{30\Omega}$ (V) | $V_{50\Omega}$ | $V_{100\Omega}$ | $V_{30\Omega} + V_{50\Omega} + V_{100\Omega}$ (V) |
|-------------|------------|--------------------|----------------|-----------------|---|
| Theoretical | 100        | 16.63V             | 27.8V          | 55.6V           | 100.05  |
| PRACTICAL   | 100        | 16.7V              | 27.8V          | 55.6            | 100.1   |

EXPT: 1

### VERIFICATION OF KIRCHOFF'S VOLTAGE LAW AND KIRCHOFF'S CURRENT LAW

#### AIM:

To verify Kirchhoff's voltage law for loops and Kirchhoff's current law for loops following circuit.

#### APPARATUS

#### REQUIRED:

Laptop with Proteus software

#### THEORY:

According to Kirchhoff's Voltage Law: Sum of potential rises are equal to sum of potential drops in a loop.

In loop 1 by KVL:

$$V = V_1 + V_2 + V_3 \quad (1)$$

$$100 = IR_1 + IR_2 + IR_3$$



$$R_{eq} = R_1 + R_2 + R_3$$

$$R_{eq} = 180\Omega$$

$$I = \frac{V}{R_{eq}}$$

$$= \frac{100}{180} = 0.556A$$

# CIRCUIT DIAGRAM

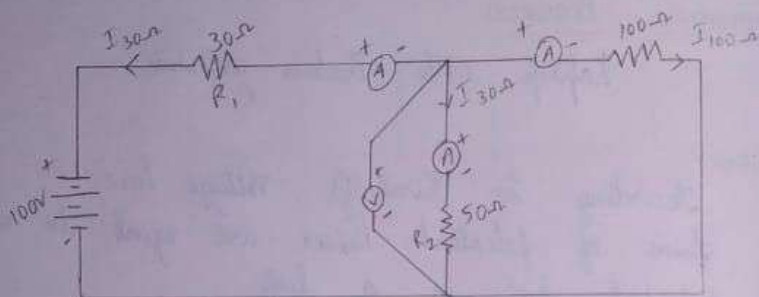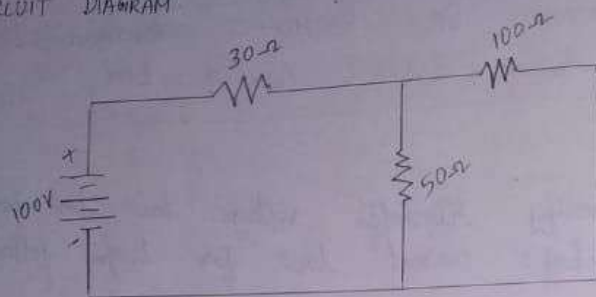

## TABULATION:

| KCL         | $I_{30\Omega}$ | $I_{50\Omega}$ | $I_{100\Omega}$ | $V_A$  |
|-------------|----------------|----------------|-----------------|--------|
| Theoretical | -1.58A         | 1.05A          | 0.53A           | 52.63V |
| Practical   | +1.58A         | +1.05A         | +0.53A          | 52.63V |

$$V_1 = V_{30\Omega} = IR_1 = 0.556 \times 30 = 16.68V$$

$$V_2 = V_{50\Omega} = IR_2 = 0.556 \times 50 = 27.8V$$

$$V_3 = V_{100\Omega} = IR_3 = 0.556 \times 100 = 55.6V$$

Substitute  $V_1$ ,  $V_2$  and  $V_3$  value in ①

$$100 = 16.68 + 27.8 + 55.6 = 100V = 100V$$

Hence, proved.

## Kirchoff's Current Law:

In a junction, incoming current is equal to outgoing current.

At node A:

$$I_{30\Omega} + I_{50\Omega} + I_{100\Omega} = 0$$


$$V = 100/30 + V/50 + V/100 = 0$$


$$V = [1/30 + 1/50 + 1/100] - \frac{100}{30} = 0$$

$$V = [0.633] - 3.333 = 0$$

$$V = \frac{3.333}{0.633} = 52.63V$$
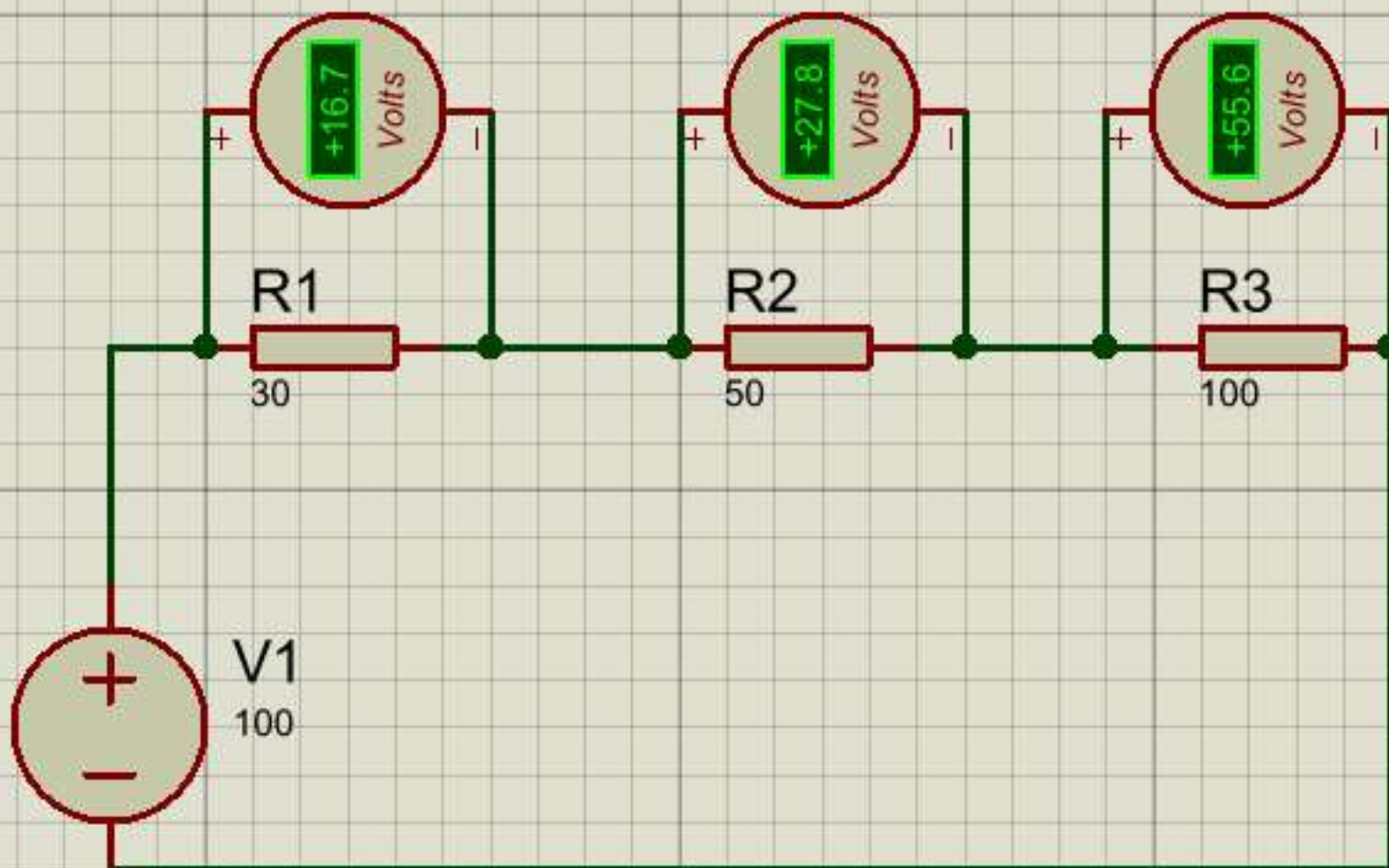
$$I_{30\Omega} = \frac{V-100}{30} = \frac{52.63}{30} = 1.58A$$



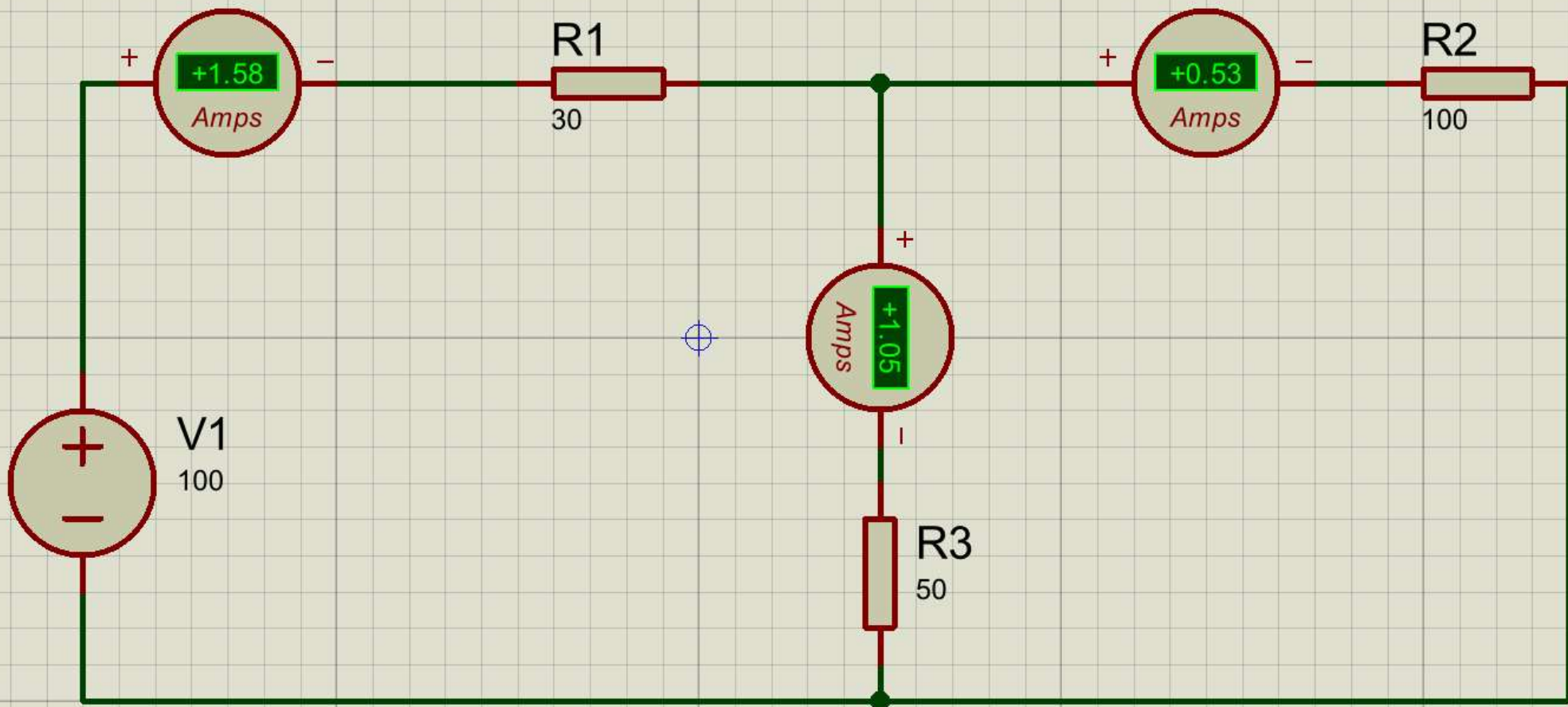

$$I_{50\Omega} = V/50 = \frac{52.63}{50} = 1.05A$$

$$I_{100\Omega} = V/100 = \frac{52.63}{100} = 0.50A$$

At node A

$$I_{30\Omega} + I_{50\Omega} + I_{100\Omega} = 0$$

$$-1.58A + 1.05A + 0.53A = 0$$

Hence, proved.

RESULT:

Thus the Kirchhoff's Voltage law and Kirchhoff's Current law has been verified successfully.